

Class : BE 6

Roll. No : 42260


Assignment No. : 1

Assignment Name : Full Adder

Date Of Performance : 18/8/21

Assignment: Write a VHDL Program to Model a Full Adder. Synthesize the model for the target PLD. Simulate the model using a TestBench. Implement it on the target PLD

Block Diagram:

 

Truth Table:

Inputs			Outputs	
A	B	C <sub>in</sub>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Main VHDL Program:

**Behavioural**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

use IEEE.STD\_LOGIC\_unsigned.ALL;

entity fullbehavior is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

CIN : in STD\_LOGIC;

SUM : out STD\_LOGIC;

COUT : out STD\_LOGIC);

end fullbehavior;

architecture Behavioral of fullbehavior is

signal temp: std\_logic\_vector(1 downto 0);

begin

process(A,B,CIN)

begin

temp <= ('0' & A) + ('0' & B) + ('0' & CIN) ;

end process;

SUM <= temp(0);

COUT <= temp(1);

end Behavioral;

### **Dataflow**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fulladderlogic is
```

```
    Port ( A : in  STD_LOGIC;
```

```
           B : in  STD_LOGIC;
```

```
           CIN : in  STD_LOGIC;
```

```
           SUM : out STD_LOGIC;
```

```
           COUT : out STD_LOGIC);
```

```
end fulladderlogic;
```

```
architecture Behavioral_Sampreeti of fulladderlogic is
```

```
begin
```

```
SUM <= ((A XOR B) XOR CIN);
```

```
COUT <= (A AND B) OR (B AND CIN) OR (A AND CIN);
```

```
end Behavioral_Sampreeti;
```

### **Structural**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity halfadderlogic is
```

```
    Port ( P : in  STD_LOGIC;
```

```
           Q : in  STD_LOGIC;
```

```
           S : out STD_LOGIC;
```

```
           C : out STD_LOGIC);
```

```
end halfadderlogic;
```

```
architecture Behavioral_Sampreeti of halfadderlogic is
```

```
begin
```

```
S <= P xor Q;
```

```
C <= P AND Q;
```

```
end Behavioral_Sampreeti;
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity orgate is
```

```
    Port ( X : in  STD_LOGIC;
```

```
           Y : in  STD_LOGIC;
```

```
           Z : out STD_LOGIC);
```

```
end orgate;
```

```
architecture Behavioral of orgate is
```

```
begin
```

```
Z <= X OR Y;
```

```
end Behavioral;
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

entity fulladder is

```
    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           CIN : in  STD_LOGIC;
           SUM : out STD_LOGIC;
           COUT : out STD_LOGIC);
```

end fulladder;

architecture Behavioral\_Sampreeti of fulladder is

component halfadderlogic

```
    Port ( P : in  STD_LOGIC;
           Q : in  STD_LOGIC;
           S : out STD_LOGIC;
           C : out STD_LOGIC);
```

end COMPONENT;

component orgate

```
    Port ( X : in  STD_LOGIC;
           Y : in  STD_LOGIC;
           Z : out STD_LOGIC);
```

end COMPONENT;

```
signal S1,C1,C2:STD_LOGIC;
```

```
begin
```

```
m1: halfadderlogic port map(A,B,S1,C1);
```


```
m2: halfadderlogic port map(S1,CIN,SUM,C2);
```


```
--COUT <= C1 OR C2; mixed
```

```
m3: orgate port map(C1,C2,COUT);
```


```
end Behavioral_Sampreeti;
```

RTL Schematic:

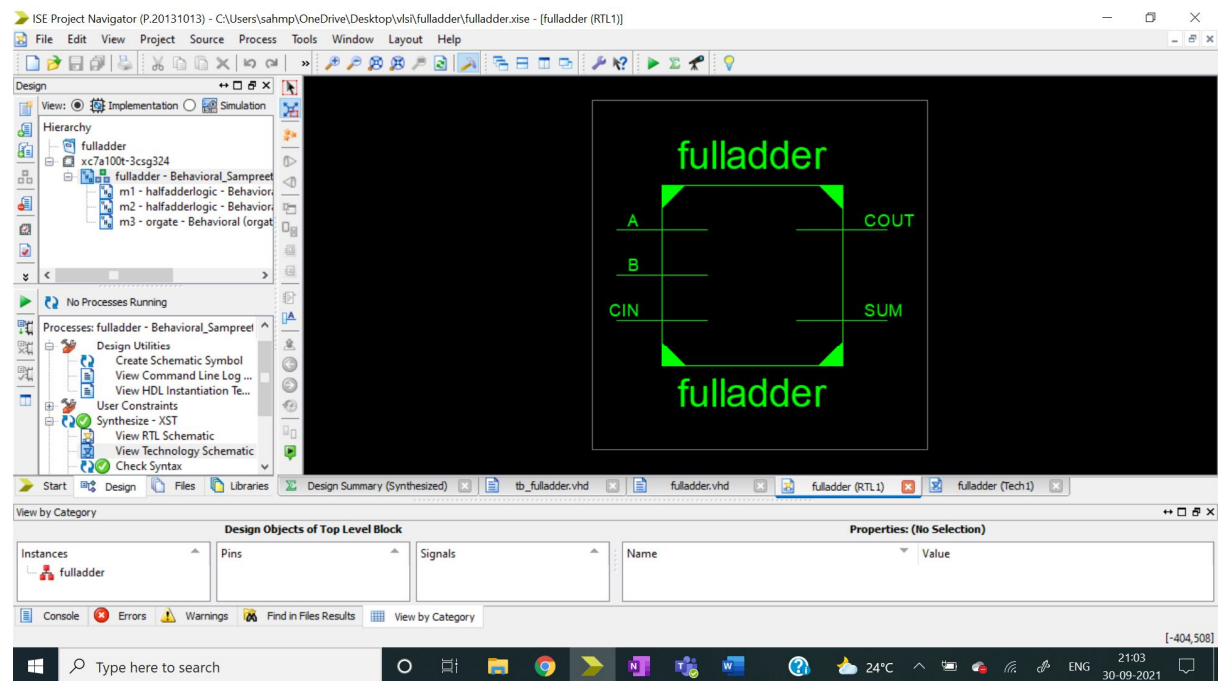

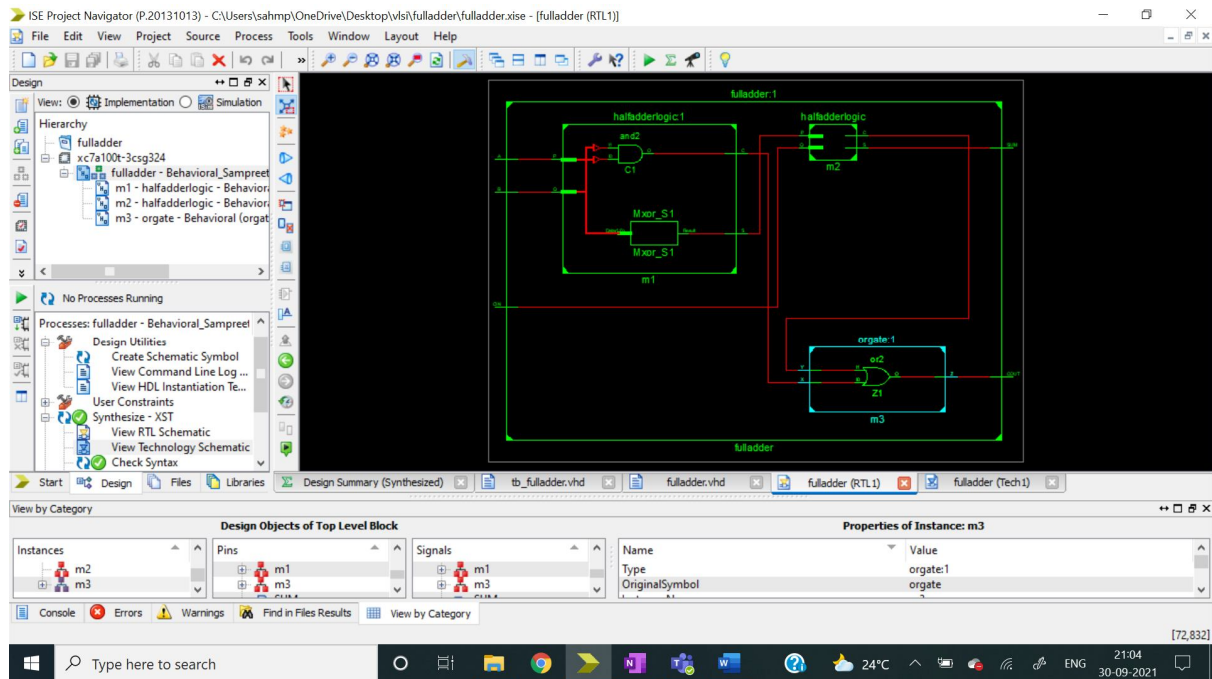

## Technology Schematic:

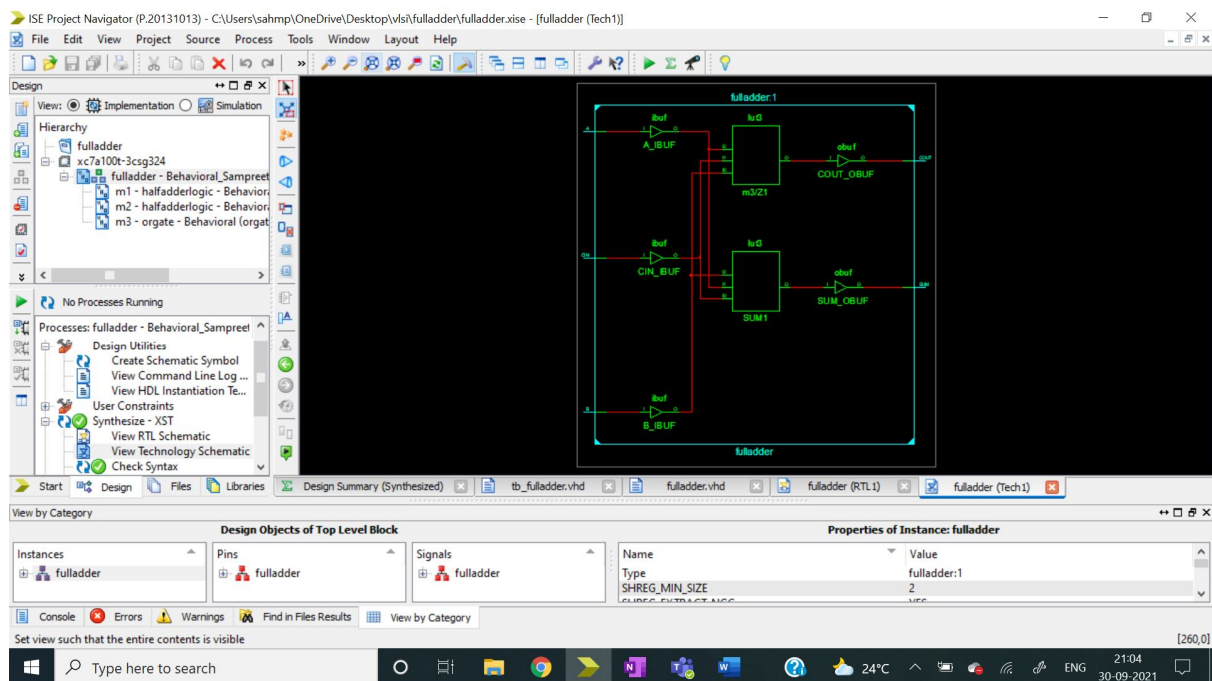

## Synthesis Report

### a) Device Utilisation Summary

Top Level Output File Name : fulladder.ngc

Primitive and Black Box Usage:

# BELS : 2

# LUT3 : 2  
# IO Buffers : 5  
# IBUF : 3  
# OBUF : 2

Device utilization summary:

-----  
Selected Device : 7a100tcsg324-3

Slice Logic Utilization:

Number of Slice LUTs: 2 out of 63400 0%  
Number used as Logic: 2 out of 63400 0%

Slice Logic Distribution:

Number of LUT Flip Flop pairs used: 2  
Number with an unused Flip Flop: 2 out of 2 100%  
Number with an unused LUT: 0 out of 2 0%  
Number of fully used LUT-FF pairs: 0 out of 2 0%  
Number of unique control sets: 0

IO Utilization:

Number of IOs: 5  
Number of bonded IOBs: 5 out of 210 2%

Specific Feature Utilization:

## b) Timing Report

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT  
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----  
No clock signals found in this design

Asynchronous Control Signals Information:

-----  
No asynchronous control signals found in this design

Timing Summary:

-----  
Speed Grade: -3

Minimum period: No path found

Minimum input arrival time before clock: No path found



Maximum output required time after clock: No path found

Maximum combinational path delay: 0.893ns

Timing Details:

-----

All values displayed in nanoseconds (ns)

Testbench Program:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY tb_fulladder IS
```

```
END tb_fulladder;
```

```
ARCHITECTURE behavior OF tb_fulladder IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT fulladder
```

```
PORT(
```

```
    A : IN std_logic;
```

```
    B : IN std_logic;
```

```
    CIN : IN std_logic;
```

```
    SUM : OUT std_logic;
```

```
    COUT : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic := '0';
signal B : std_logic := '0';
signal CIN : std_logic := '0';
```

```
--Outputs
```

```
signal SUM : std_logic;
```

```
signal COUT : std_logic;
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: fulladder PORT MAP (
```

```
    A => A,
```

```
    B => B,
```

```
    CIN => CIN,
```

```
    SUM => SUM,
```

```
    COUT => COUT
```

```
);
```

```
-- Clock process definitions
```

```
-- <clock>_process :process
```

```
-- begin
```

```
--             <clock> <= '0';
```

```
--             wait for <clock>_period/2;
```

```
--             <clock> <= '1';
```

```
--             wait for <clock>_period/2;
```

```
-- end process;
```

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    --wait for <clock>_period*10;

    -- insert stimulus here

        A <='0';
    B <='0';
    CIN <='0';
    wait for 100 ns;

        A <='0';
    B <='0';
    CIN <='1';
    wait for 100 ns;

        A <='0';
    B <='1';
    CIN <='0';
    wait for 100 ns;

        A <='0';
    B <='1';
    CIN <='1';
    wait for 100 ns;

        A <='1';
    B <='0';
    CIN <='0';
    wait for 100 ns;

```

```

A <='1';

B <='0';

CIN <='1';

wait for 100 ns;

```

```

A <='1';

B <='1';

CIN <='0';

wait for 100 ns;

A <='1';

B <='1';

CIN <='1';

wait for 100 ns;

```


```

end process;

```

END;

Isim Waveforms:

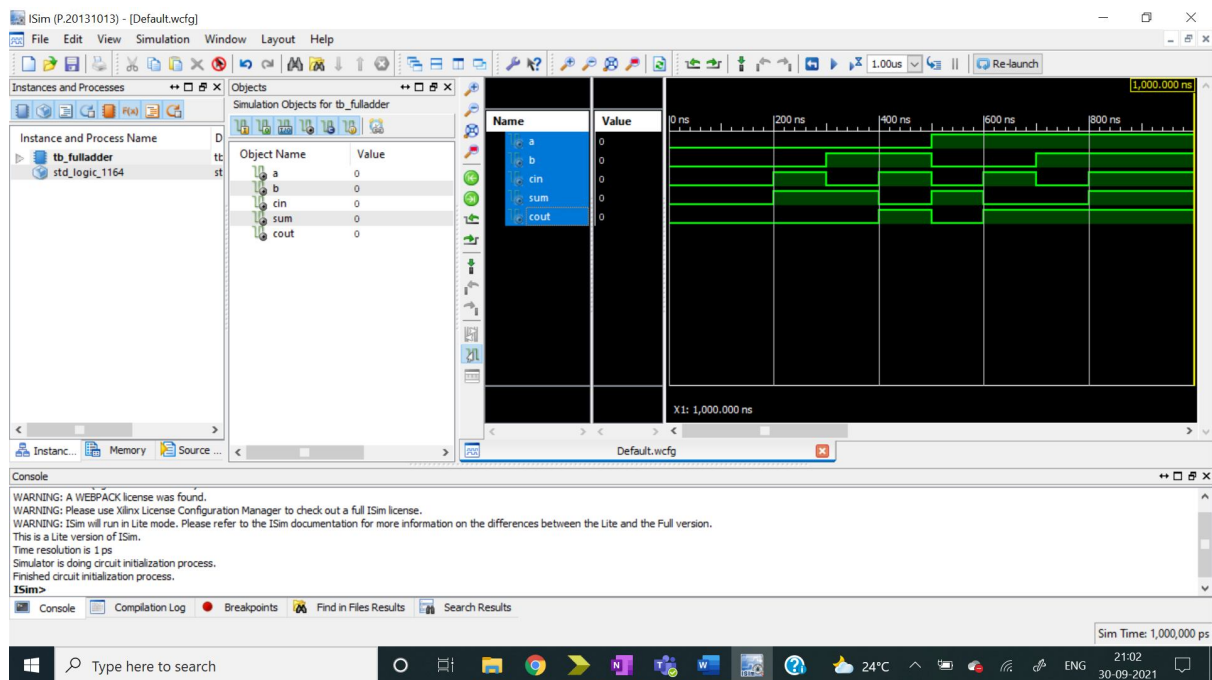

Conclusion:

Thus we have :

- 1) Modeled Full Adder using Dataflow,Behavioral,Structural and Mixed Modeling Styles.
- 2) Observed following Schematics : RTL & Technology Schematics generated Post-Synthesis.
- 3) Interpreted Device Utilisation Summary in terms of LUTs , SLICES , IOBs , Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency .
- 5) Written a TESTBENCH to verify the functionality of Full Adder & verified the functionality as per the TRUTH-TABLE ,by observing ISIM Waveforms.
- 6) Prototyped the FPGA XC3S250EPQ208-5 to realize Full Adder & verified its operation by giving suitable input combinations