

Class : BE 6

Roll. No : 42260



Assignment No. : 1

Assignment Name : 4 bit ALU

Date Of Performance : 20/9/21

Assignment: Write a VHDL Program to Model a 4 bit ALU. Synthesize the model for the target PLD. Simulate the model using a TestBench. Implement it on the target PLD

Block Diagram:

 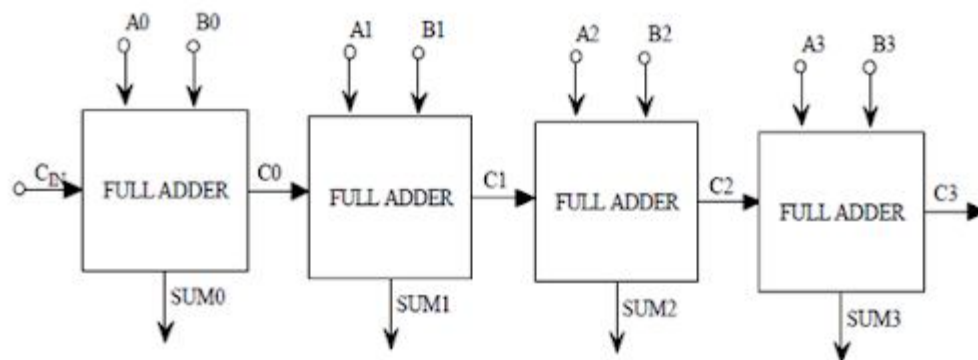

Truth Table:

Selection Input			Operation Performed
0	0	0	A + B
0	0	1	A - B
0	1	0	A - 1
0	1	1	A + 1
1	0	0	A and B
1	0	1	A or B
1	1	0	not A
1	1	1	A xor B

Main VHDL Program:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity singlebit is
```

```
    Port ( P : in  STD_LOGIC;
```

```
          Q : in  STD_LOGIC;
```

```
          CI : in  STD_LOGIC;
```

```
          SUM : out STD_LOGIC;
```

```
          CO : out STD_LOGIC);
```

```
end singlebit;
```

```
architecture Behavioral_single of singlebit is
```

```
begin
```

```
SUM <= ((P XOR Q) XOR CI);
```

```
CO <= (P AND Q) OR (Q AND CI) OR (P AND CI);
```

```
end Behavioral_single;
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fourbitrippleadder is
```

```
PORT( X : IN  std_logic_vector(3 downto 0);
```

```
      Y : IN  std_logic_vector(3 downto 0);
```

```
      CIN : IN  std_logic;
```

```
      COUT : OUT std_logic;
```

```
      S : OUT  std_logic_vector(3 downto 0));
```

```
end fourbitrippleadder;
```

```
architecture Behavioral_Sampreeti of fourbitrippleadder is
```

```
component singlebit
```

```

Port ( P : in STD_LOGIC;
      Q : in STD_LOGIC;
      CI : in STD_LOGIC;
      SUM : out STD_LOGIC;
      CO : out STD_LOGIC);
end COMPONENT;

```

```

signal TEMP0,TEMP1,TEMP2:STD_LOGIC;

```

```

begin

```

```

m1: singlebit port map(X(0),Y(0),CIN,S(0),TEMP0);
m2: singlebit port map(X(1),Y(1),TEMP0,S(1),TEMP1);
m3: singlebit port map(X(2),Y(2),TEMP1,S(2),TEMP2);
m4: singlebit port map(X(3),Y(3),TEMP2,S(3),COUT);

```

```

end Behavioral_Sampreeti;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

```

```

entity aluprocess is

```

```

Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
      b : in STD_LOGIC_VECTOR(3 downto 0);
      sel : in STD_LOGIC_VECTOR (2 downto 0);
      out_alu : out STD_LOGIC_VECTOR (3 downto 0);
      carry : out STD_logic);
end aluprocess;

```

architecture Behavioral_alu of aluprocess is

component fourbitrippleadder

PORT(X : IN std_logic_vector(3 downto 0);

Y : IN std_logic_vector(3 downto 0);

CIN : IN std_logic;

COUT : OUT std_logic;

S : OUT std_logic_vector(3 downto 0));

end component;

signal hold1: std_logic_vector(3 downto 0);

signal hold2: std_logic_vector(3 downto 0);

signal carry1: std_logic;

signal carry2: std_logic;

begin

f1: fourbitrippleadder port map(a,b,'0',carry1,hold1);

f2: fourbitrippleadder port map(a,"0001",'0',carry2,hold2);

with sel select out_alu <=

hold1 when "000" ,

a - b when "001" ,

a - 1 when "010" ,

hold2 when "011" ,

a and b when "100" ,

a or b when "101" ,

not a when "110" ,

a xor b when "111" ;

with sel select carry <=

carry1 when "000" ,


```

        '0' when "001" ,
        '0' when "010" ,
        carry2 when "011" ,
        '0' when "100" ,
        '0' when "101" ,
        '0' when "110" ,
        '0' when "111" ;

end Behavioral_alu;

```

RTL Schematic:

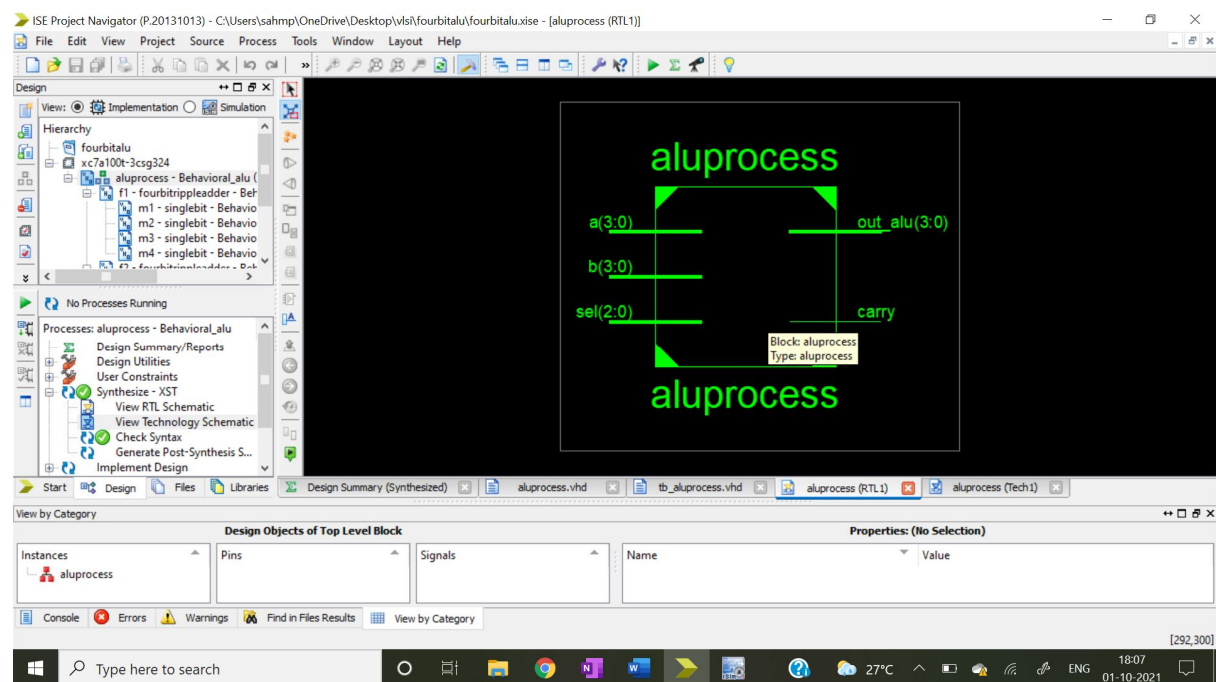

#	LUT2	:	1
#	LUT3	:	2
#	LUT4	:	6
#	LUT5	:	4
#	LUT6	:	8
#	IO Buffers	:	16
#	IBUF	:	11
#	OBUF	:	5

Device utilization summary:

Selected Device : 7a100tcsg324-3

Slice Logic Utilization:

Number of Slice LUTs:	21	out of	63400	0%
Number used as Logic:	21	out of	63400	0%

Slice Logic Distribution:

Number of LUT Flip Flop pairs used:	21			
Number with an unused Flip Flop:	21	out of	21	100%
Number with an unused LUT:	0	out of	21	0%
Number of fully used LUT-FF pairs:	0	out of	21	0%
Number of unique control sets:	0			

IO Utilization:

Number of IOs:	16			
Number of bonded IOBs:	16	out of	210	7%

Specific Feature Utilization:

b) Timing Report

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.
FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

No clock signals found in this design

Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -3

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 3.022ns

Timing Details:

All values displayed in nanoseconds (ns)

Testbench Program:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
use IEEE.STD_LOGIC_unsigned.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY tb_aluprocess IS
```

```
END tb_aluprocess;
```

```
ARCHITECTURE behavior OF tb_aluprocess IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT aluprocess
```

```
PORT(
```

```
    a : IN std_logic_vector(3 downto 0);
```

```
    b : IN std_logic_vector(3 downto 0);
```

```
    sel : IN std_logic_vector(2 downto 0);
```

```
    out_alu : OUT std_logic_vector(3 downto 0);
```

```
    carry : OUT std_logic
```

```
);
```



```
END COMPONENT;
```

```
--Inputs
```

```
signal a : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal b : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal sel : std_logic_vector(2 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal out_alu : std_logic_vector(3 downto 0);
```

```
signal carry : std_logic;
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
-- constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: aluprocess PORT MAP (
```

```
    a => a,
```

```
    b => b,
```

```
    sel => sel,
```

```
    out_alu => out_alu,
```

```
    carry => carry
```

```
);
```

```
-- Clock process definitions
```

```
-- <clock>_process :process
```

```
-- begin
```

```
--             <clock> <= '0';
```

```


--          wait for <clock>_period/2;
--          <clock> <= '1';
--          wait for <clock>_period/2;
-- end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

a <= "1001";
b <= "1111";
sel <= "000";
wait for 100 ns;
sel <= "001";
wait for 100 ns;
sel <= "010";
wait for 100 ns;
sel <= "011";
wait for 100 ns;
sel <= "100";
wait for 100 ns;
sel <= "101";
wait for 100 ns;
sel <= "110";
wait for 100 ns;
sel <= "111";
end process;

END;
```

Isim Waveforms:

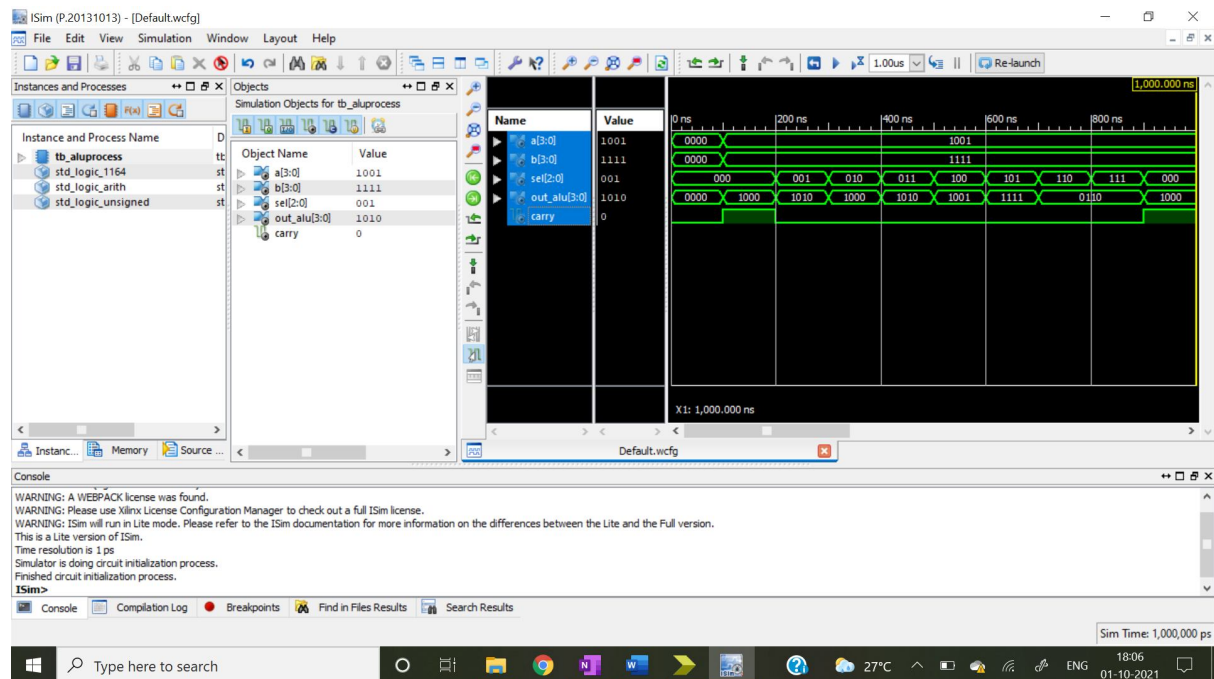

Pin Locking Report: Attached separately

Conclusion:

Thus we have :

- 1) Modeled a 4 bit ALU using Behavioral Modeling Style.
- 2) Observed following Schematics : RTL & Technology Schematics generated Post-Synthesis.
- 3) Interpreted Device Utilisation Summary in terms of LUTs , SLICES , IOBs , Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency .
- 5) Written a TESTBENCH to verify the functionality of 4 bit ALU & verified the functionality as per the TRUTH-TABLE ,by observing ISIM Waveforms.
- 6) Used PlanAhead Editor for pin-locking.
- 7) Prototyped the FPGA XC3S250EPQ208-5 to realize 4 bit ALU & verified its operation by giving suitable input combinations