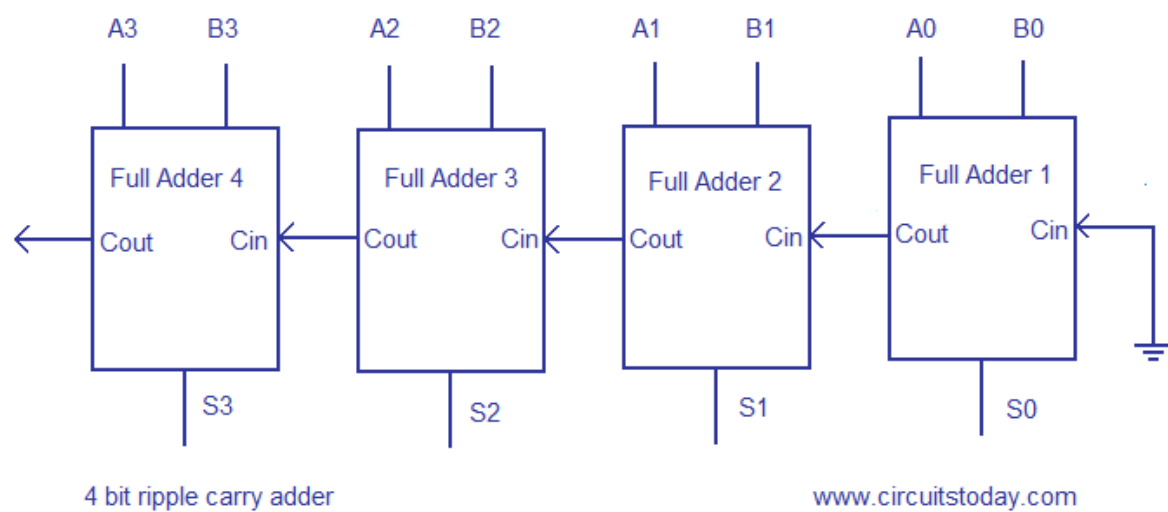


Date Of Performance : 25/8/21

Assignment: Write a VHDL Program to Model a 4 bit ripple carry adder. Synthesize the model for the target PLD. Simulate the model using a TestBench. Implement it on the target PLD


Block Diagram:



Truth Table:

[illegible]

Inputs			Outputs	
A	B	Cin	Cout	S
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

 

1 bit full adder truth table & schematic

Main VHDL Program:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity singlebit is

```
Port ( P : in STD_LOGIC;
```

```
      Q : in STD_LOGIC;
```

```
      CI : in STD_LOGIC;
```

```
      SUM : out STD_LOGIC;
```

```
      CO : out STD_LOGIC);
```

```
end singlebit;
```

architecture Behavioral of singlebit is

```
begin
```

```
SUM <= ((P XOR Q) XOR CI);
```

```
CO <= (P AND Q) OR (Q AND CI) OR (P AND CI);
```

```
end Behavioral;
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx primitives in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
entity fourbitrippleadder is
```

```
PORT( A : IN std_logic_vector(3 downto 0);
```

```
      B : IN std_logic_vector(3 downto 0);
```

```
      CIN : IN std_logic;
```

```
      COUT : OUT std_logic;
```

```
      S : OUT std_logic_vector(3 downto 0));
```

```
-- Port ( A0 : in STD_LOGIC;
```

```
--      A1 : in STD_LOGIC;
```

```
--      A2 : in STD_LOGIC;
```

```
--      A3 : in STD_LOGIC;
```

```
--      B0 : in STD_LOGIC;
```

```
--      B1 : in STD_LOGIC;
```

```
--      B2 : in STD_LOGIC;
```

```
--      B3 : in STD_LOGIC;
```

```

--      CIN : in  STD_LOGIC;
--      COUT : out STD_LOGIC;
--      S0 : out  STD_LOGIC;
--      S1 : out  STD_LOGIC;
--      S2 : out  STD_LOGIC;
--      S3 : out  STD_LOGIC);
end fourbitrippleadder;

```

architecture Behavioral\_Sampreeti of fourbitrippleadder is

component singlebit

```

    Port ( P : in  STD_LOGIC;
          Q : in  STD_LOGIC;
          CI : in  STD_LOGIC;

          SUM : out STD_LOGIC;
          CO : out STD_LOGIC);
end COMPONENT;

```

signal TEMP0,TEMP1,TEMP2:STD\_LOGIC;

begin



```

m1: singlebit port map(A(0),B(0),CIN,S(0),TEMP0);
m2: singlebit port map(A(1),B(1),TEMP0,S(1),TEMP1);
m3: singlebit port map(A(2),B(2),TEMP1,S(2),TEMP2);
m4: singlebit port map(A(3),B(3),TEMP2,S(3),COUT);


```

end Behavioral\_Sampreeti;

## RTL Schematic:

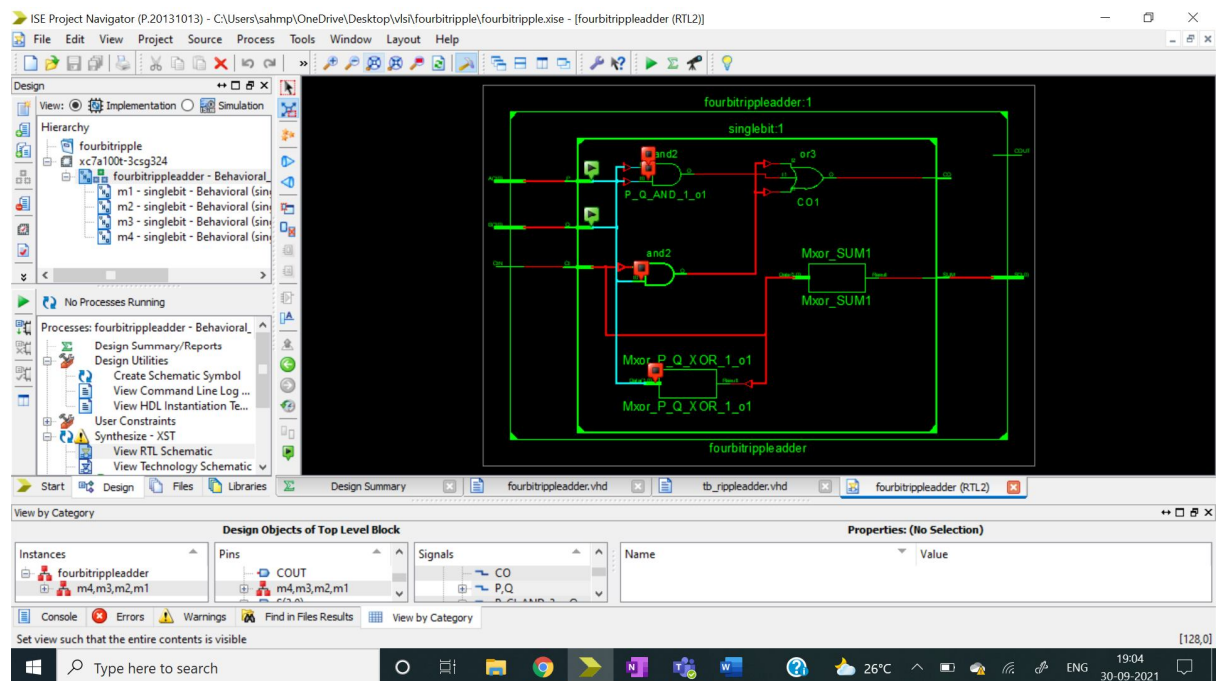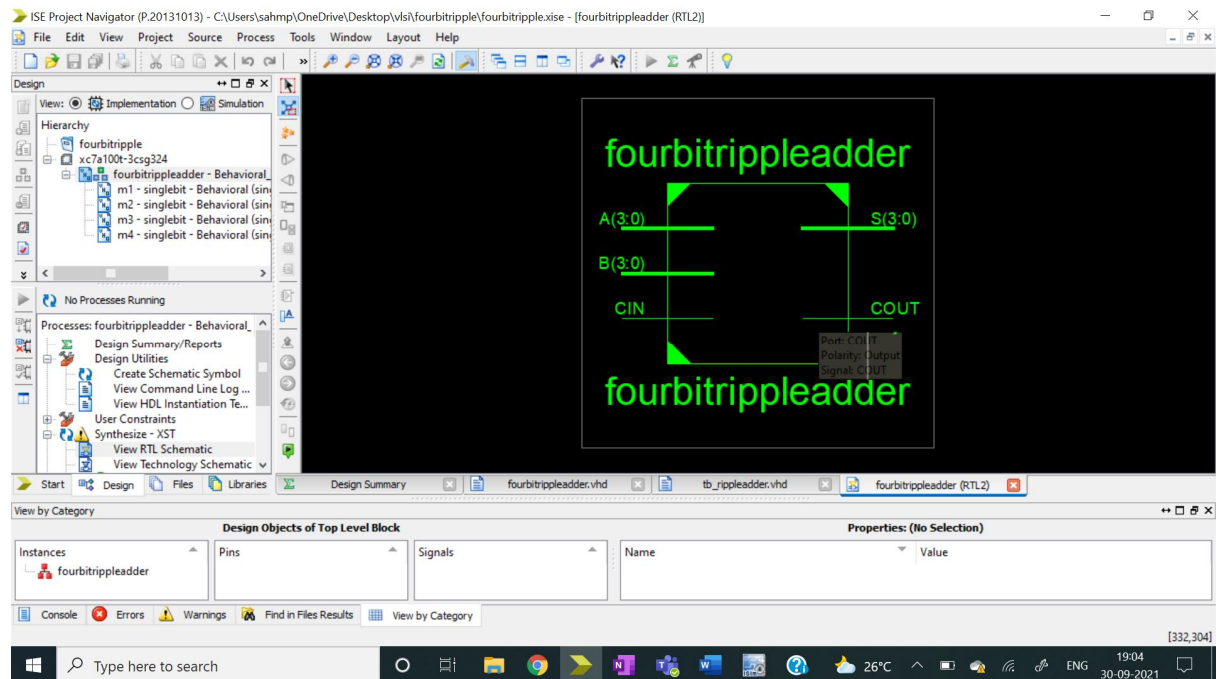

## Technology Schematic:

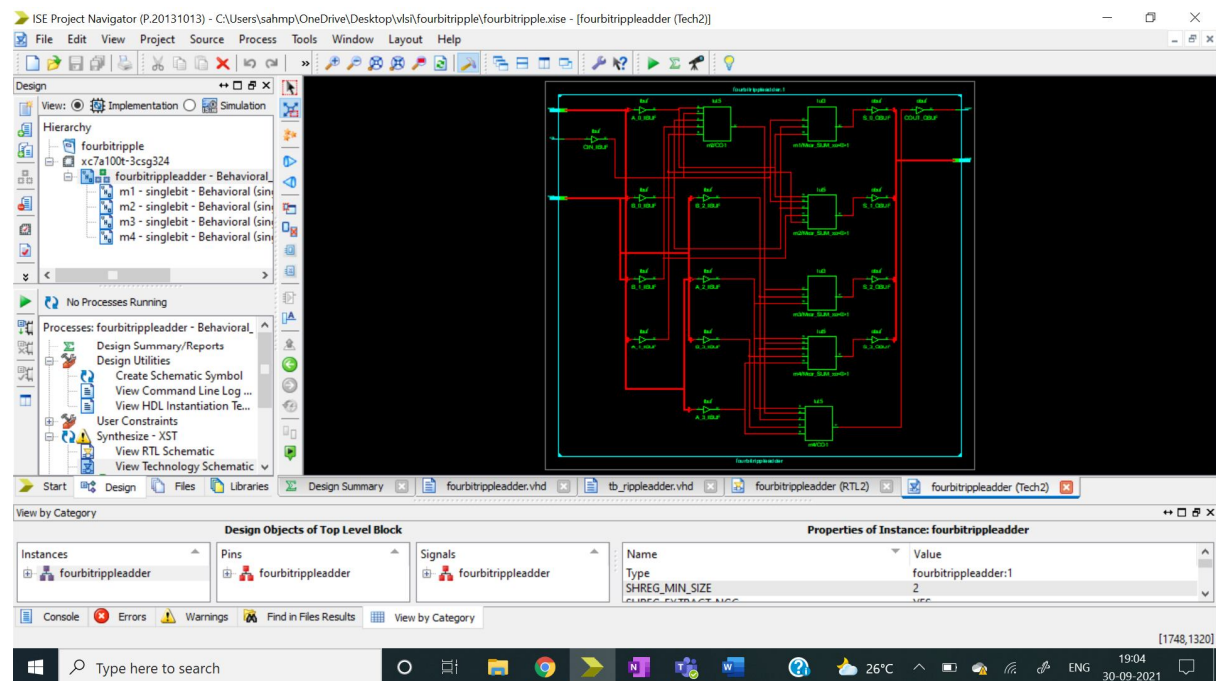

## Synthesis Report

### a) Device Utilisation Summary

Top Level Output File Name : fourbitrippleadder.ngc

Primitive and Black Box Usage:

-----

# BELS	: 6
# LUT3	: 2
# LUT5	: 4
# IO Buffers	: 14
# IBUF	: 9
# OBUF	: 5

Device utilization summary:

-----

Selected Device : 7a100tcsg324-3

Slice Logic Utilization:

Number of Slice LUTs:	6 out of 63400	0%
Number used as Logic:	6 out of 63400	0%

Slice Logic Distribution:

Number of LUT Flip Flop pairs used: 6  
Number with an unused Flip Flop: 6 out of 6 100%  
Number with an unused LUT: 0 out of 6 0%  
Number of fully used LUT-FF pairs: 0 out of 6 0%  
Number of unique control sets: 0

IO Utilization:

Number of IOs: 14  
Number of bonded IOBs: 14 out of 210 6%

Specific Feature Utilization:

b) Timing Report

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.  
FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT  
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----

No clock signals found in this design

Asynchronous Control Signals Information:

-----

No asynchronous control signals found in this design

Timing Summary:

-----

Speed Grade: -3

Minimum period: No path found  
Minimum input arrival time before clock: No path found  
Maximum output required time after clock: No path found  
Maximum combinational path delay: 1.551ns

Timing Details:

-----

All values displayed in nanoseconds (ns)

Testbench Program:

LIBRARY ieee;

USE ieee.std\_logic\_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY tb_rippleadder IS
```

```
END tb_rippleadder;
```

```
ARCHITECTURE behavior OF tb_rippleadder IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT fourbitrippleadder
```

```
PORT(
```

```
    A : IN  std_logic_vector(3 downto 0);
```

```
    B : IN  std_logic_vector(3 downto 0);
```

```
    CIN : IN  std_logic;
```

```
    COUT : OUT std_logic;
```

```
    S : OUT std_logic_vector(3 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal B : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal CIN : std_logic := '0';
```

```
--Outputs
```

```
signal COUT : std_logic;
```

```
signal S : std_logic_vector(3 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```



```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
    -- Instantiate the Unit Under Test (UUT)
```

```
    uut: fourbitrippleadder PORT MAP (
```

```
        A => A,
```

```
        B => B,
```

```
        CIN => CIN,
```

```
        COUT => COUT,
```

```
        S => S
```

```
    );
```

```
    -- Clock process definitions
```

```
    -- <clock>_process :process
```

```
    -- begin
```

```
    --          <clock> <= '0';
```

```
    --          wait for <clock>_period/2;
```

```
    --          <clock> <= '1';
```

```
    --          wait for <clock>_period/2;
```

```
    -- end process;
```

```
    -- Stimulus process
```

```
    stim_proc: process
```

```
    begin
```

```
        -- hold reset state for 100 ns.
```

```
        wait for 100 ns;
```

```
        A<="0010";
```

```
        B<="0010";
```

```
CIN <='0';
```

```
wait for 100 ns;
```

```
A<="1000";
```

```
B<="1000";
```

```
CIN <='0';
```

```
wait for 100 ns;
```

```
A<="1111";
```

```
B<="1111";
```

```
CIN <='1';
```


```
wait for 100 ns;
```

```
-- insert stimulus here
```

```
end process;
```

```
END;
```

Isim Waveforms:

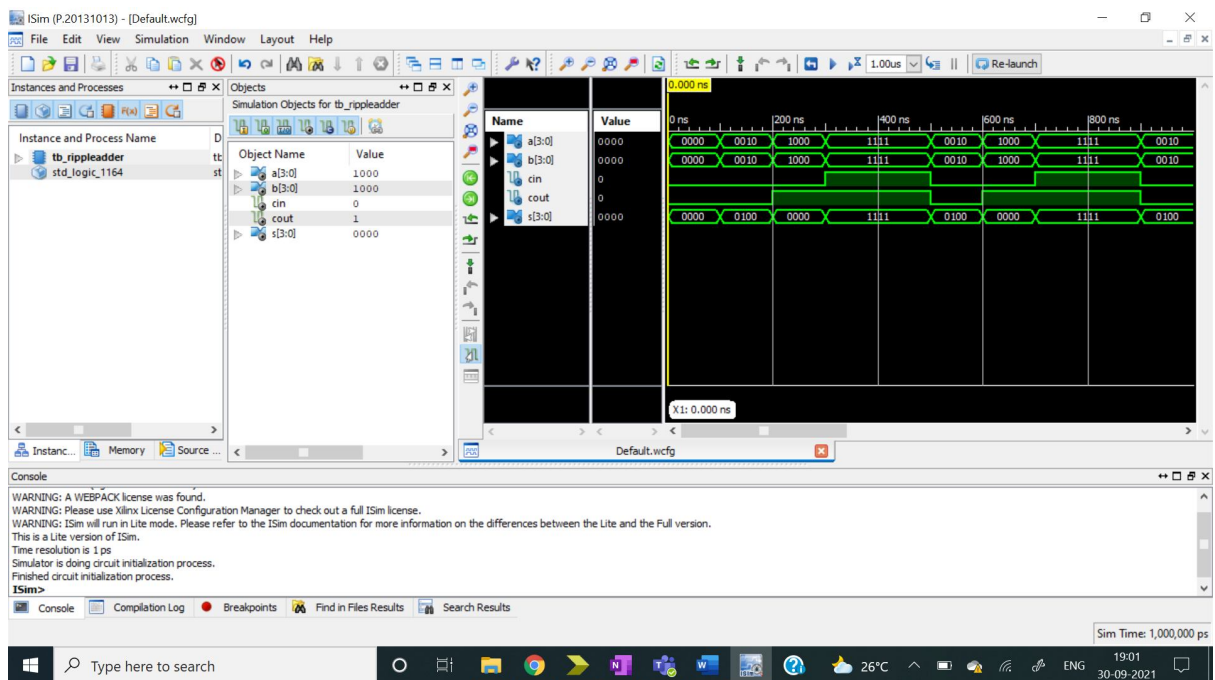

Conclusion:

Thus we have :

- 1) Modeled a 4 bit ripple carry adder using Behavioral Modeling Style.
- 2) Observed following Schematics : RTL & Technology Schematics generated Post-Synthesis.
- 3) Interpreted Device Utilisation Summary in terms of LUTs , SLICES , IOBs , Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency .
- 5) Written a TESTBENCH to verify the functionality of 4 bit ripple carry adder & verified the functionality as per the TRUTH-TABLE ,by observing ISIM Waveforms.
- 6) Prototyped the FPGA XC3S250EPQ208-5 to realize 4 bit ripple carry adder & verified its operation by giving suitable input combinations